

BME 393L Lab 1: Simple Circuit

Fenglin Chen (20823934), Jane Shen (20841468)

January 18th, 2022

In-Lab

4.1 Simulation of a VHDL code

```
library ieee;
use ieee.std_logic_1164.all;

entity First_circuit is
    port( SW:      in    std_logic_vector(3 downto 0);
          LEDG:    out   std_logic_vector(2 downto 0)
        );
end entity First_circuit;

architecture main of First_circuit is
    signal xor1, xor2, xor3:  std_logic;
    signal and1, and2, and3:  std_logic;
    signal or1:               std_logic;

begin

    xor1 <= sw(0) xor sw(2);
    and1 <= sw(0) and sw(2);
    xor2 <= sw(1) xor sw(3);
    and2 <= sw(1) and sw(3);
    xor3 <= and1 xor xor2;
    and3 <= and1 and xor2;
    or1  <= and2 or and3;
    LEDG(0) <= xor1;
    LEDG(1) <= xor3;
    LEDG(2) <= or1;

end architecture main;
```

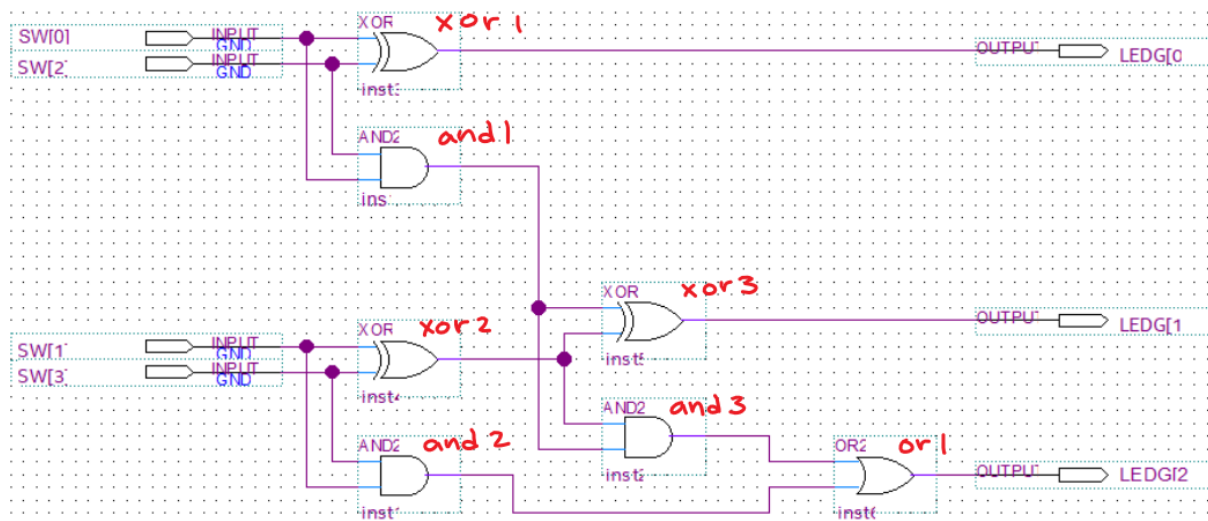


Figure 1: Gates are named and translated into the VHDL code above.

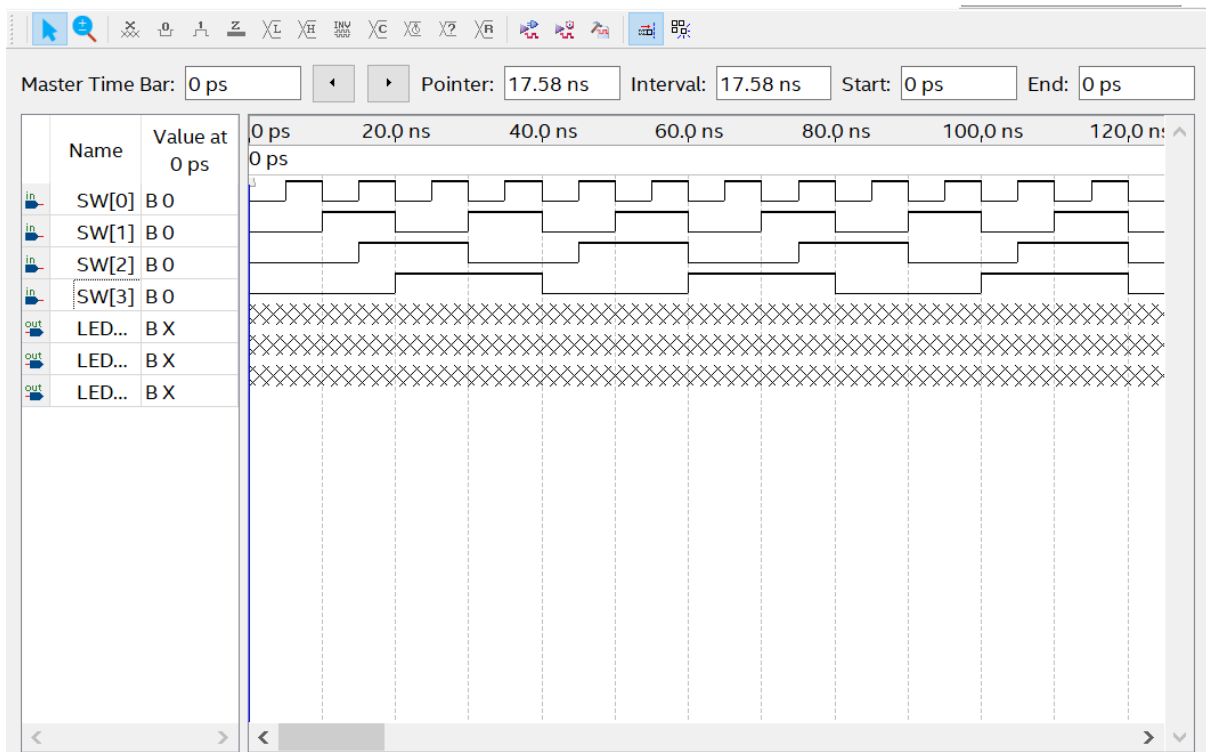


Figure 2: Inputs SW[0] to SW[3] are overwritten with 10-40 nanosecond pulses, respectively.

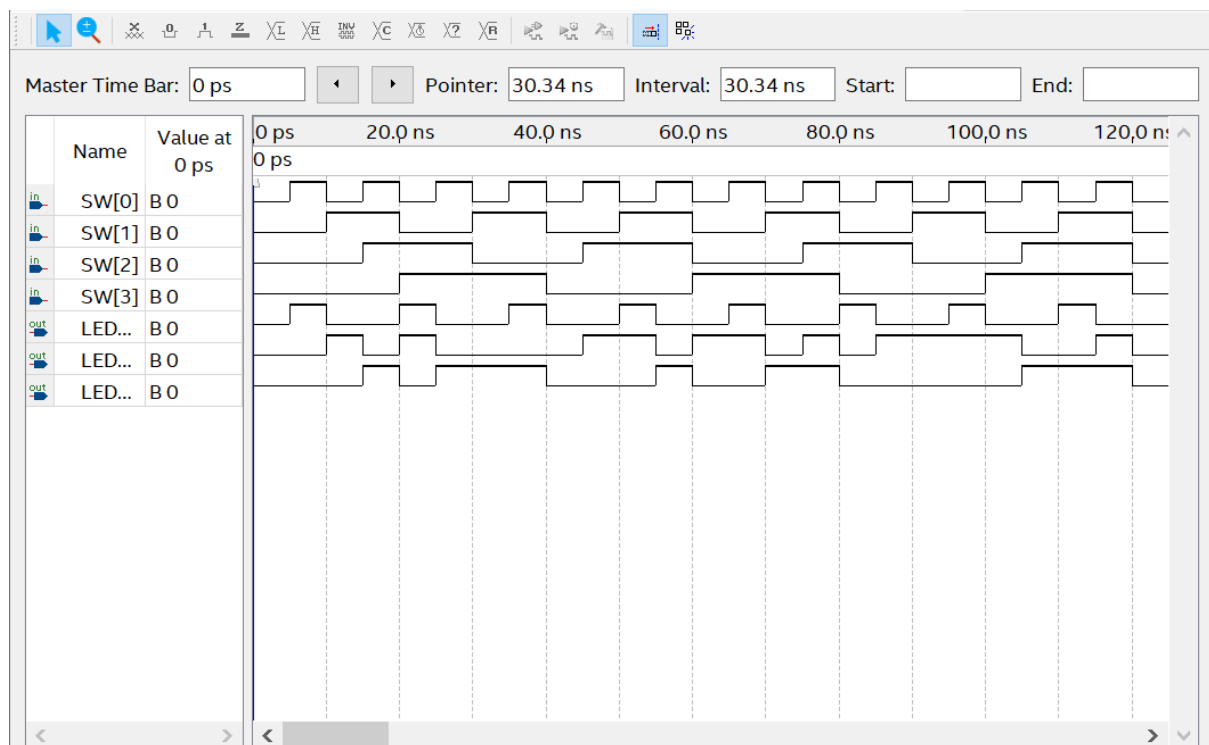


Figure 3: Outputs are generated from LED[0] to LED[2].

Table 1: Truth table for the VHDL circuit.

a(1) SW[3]	a(0) SW[2]	b(1) SW[1]	b(0) SW[0]	c(2) LEDG[2]	c(1) LEDG[1]	c(0) LEDG[0]
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

4.2. Schematic entry in digital circuits

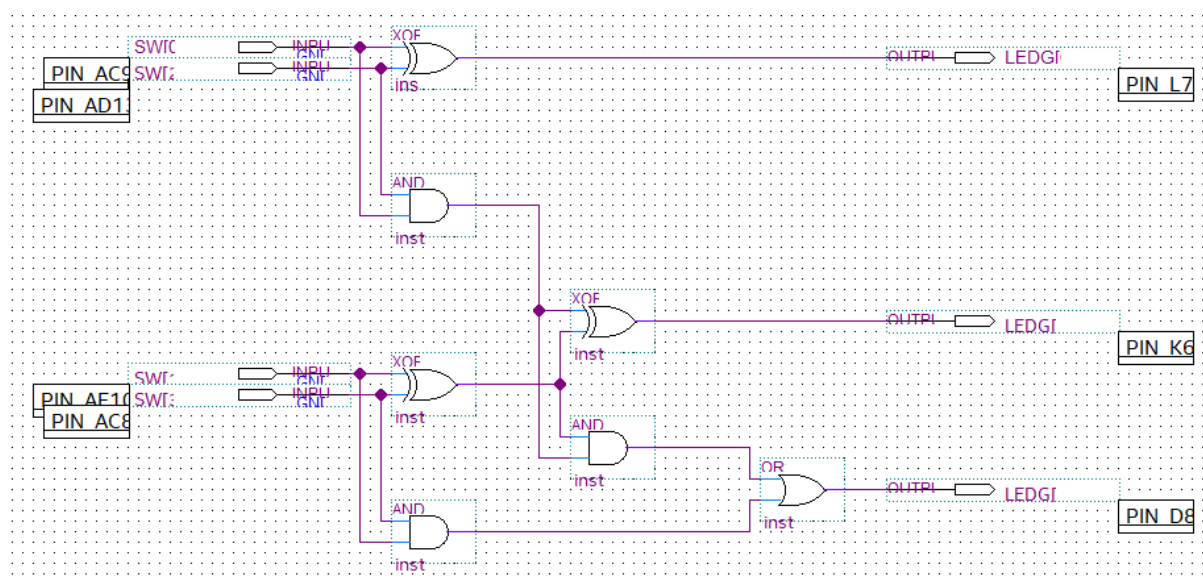


Figure 4. Simple Circuit Schematic Entry.

From top to bottom, the input pins are labeled SW[0], SW[1], SW[2], and SW[3]. In the same order, the output pins are labeled LEDG[0], LEDG[1], LEDG[2].

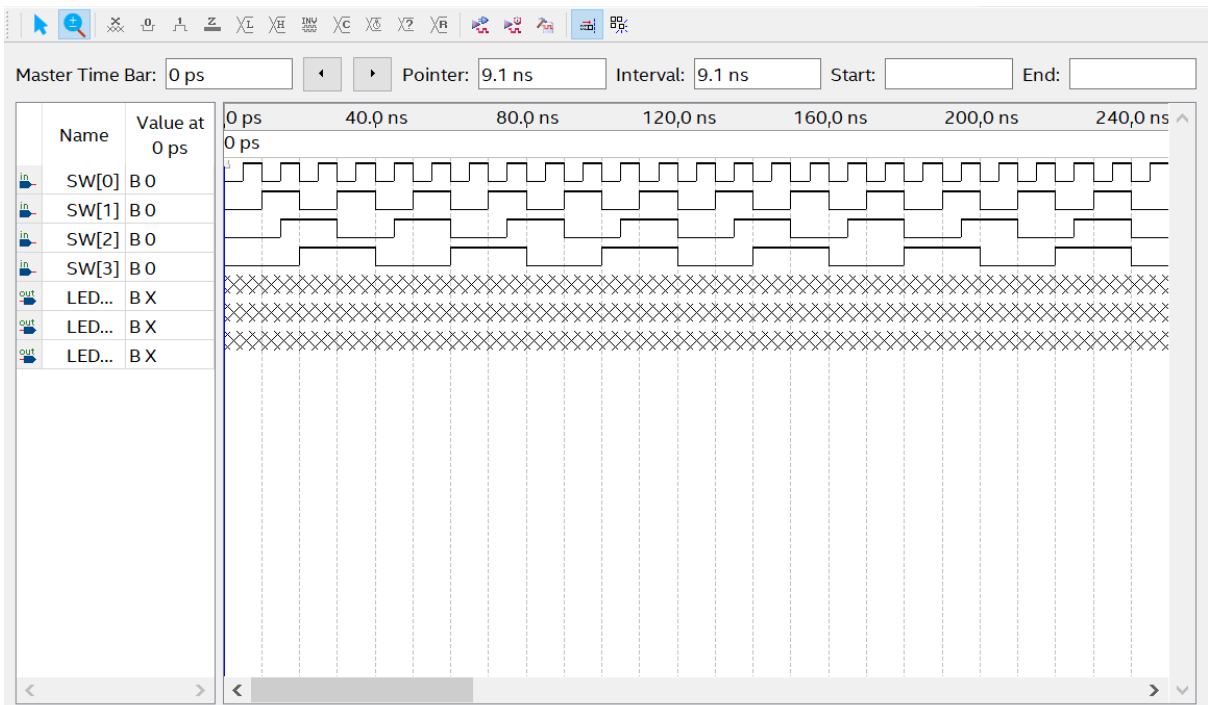


Figure 5. Waveform Input for Simple Circuit Schematic Entry.

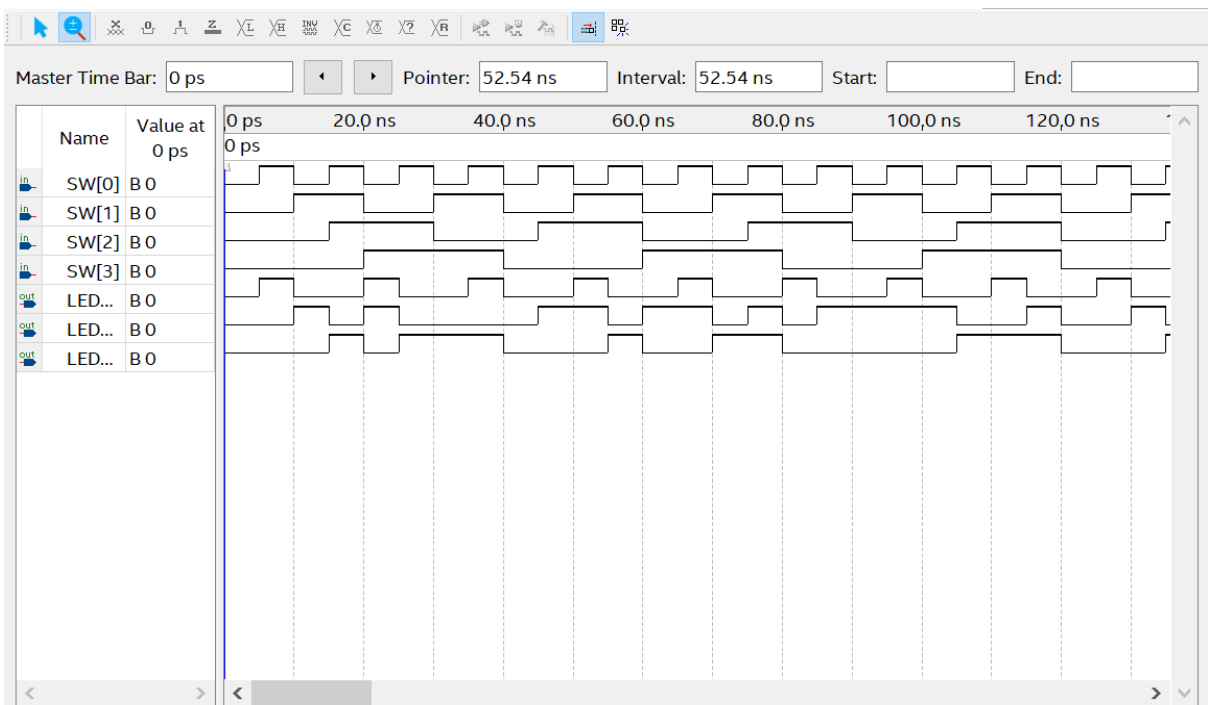


Figure 6. Simulation Results for Simple Circuit Schematic Circuit.

Table 2: Truth table for schematic entry circuit.

a(1) SW[3]	a(0) SW[2]	b(1) SW[1]	b(0) SW[0]	c(2) LEDG[2]	c(1) LEDG[1]	c(0) LEDG[0]
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

5.1. Lab Report

Table 1 from Section 4.1 and Table 2 from Section 4.2 are identical. This is also reflected in Figure 3 and Figure 6 having the same input and output waveforms. The result is expected because the circuit architecture is the same, just represented in two different formats.

Table 3: Inputs SW[0] and SW[1] are represented as Input A, SW[2] and SW[3] are presented as Input B, and the three LEDs are represented as Output C.

Input B (Decimal)	Input A (Decimal)	Output C (Decimal)
0	0	0
0	1	1
0	2	2
0	3	3

1	0	1
1	1	2
1	2	3
1	3	4
2	0	2
2	1	3
2	2	4
2	3	5
3	0	3
3	1	4
3	2	5
3	3	6

According to Table 3, Output C displays the sum of Input A and Input B. Therefore, the circuit is an adder for two two-bit binary numbers.